

## Homework 9

### 1 Problem

For circuit A in the appendix:

- Determine the current profile  $i(t)$  in response to a step-input of  $V_0$  volts using the impedance method. (Hint: find the impedance of the total circuit  $Z_{\text{circuit}}$ , solve for  $I(s)$  assuming  $V(s)$  is the desired step input, and use the inverse Laplace transform.)
- Determine the voltage profile  $v_{\text{cap}}(t)$  across the capacitor in response to a step-input of  $V_0$  volts using the impedance method. (Hint: use the ratio of  $Z_{\text{circuit}}$  to  $Z_{\text{cap}}$  to find the desired transfer function, as described in the notes.)
- If  $R = 10 \text{ ohm}$  and  $C = 15 \mu\text{F}$  how long does it take the capacitor's voltage to reach  $\approx 2 \%$  of  $V_0$ ? (Hint: determine the time constant first)

### 2 Problem

For circuit B in the appendix:

- Determine the current profile  $i(t)$  in response to a step-input of  $V_0$  volts using the impedance method.
- Determine the voltage profile  $v_{\text{ind}}(t)$  across the inductor in response to a step-input of  $V_0$  volts using the impedance method.

### 3 Problem

For circuit C in the appendix:

- Derive the transfer function

$$G_{V \rightarrow V_{\text{output}}} = \frac{V_{\text{out}}(s)}{V(s)}$$




from input voltage  $V(s)$  to output voltage  $V_{\text{out}}(s)$  (across the parallel  $RC$  connection)

- State the natural frequency and damping ratio of the circuit in terms of  $R$ ,  $C$ , and  $L$ .
- Given  $C = 10\text{E-}6$  Farads and  $L = 1\text{E-}3$  Henries select  $R$  (units of ohms) so the circuit is critically damped and state the natural frequency of the circuit in Hz.

### 4 Problem

For circuit D in the appendix. Assume that all resistors, capacitors, and inductors have the same value  $R$ ,  $C$ , and  $L$ , respectively. Find the total equivalent impedance of the circuit,  $Z_{\text{circuit}}$ . (Hint: simplify the circuit step-by-step, similar to this example [Link])

## Appendix

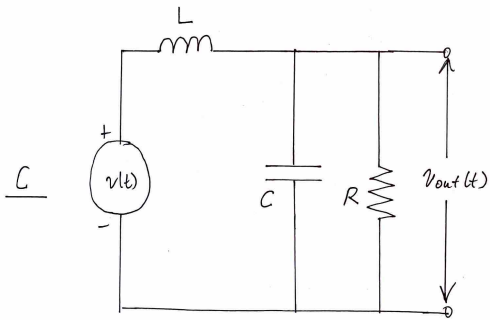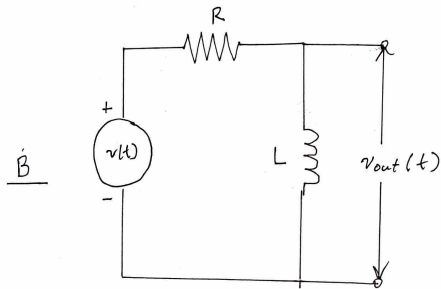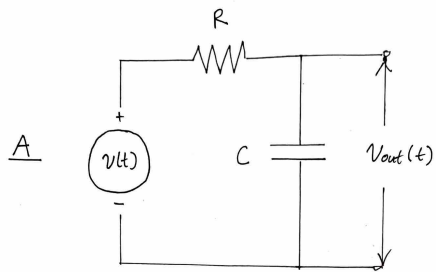

D

